UG10327

MCX E31x Hardware Design Guide Rev. 1.0 — 9 October 2025

User guide

Document information

Information	Content
Keywords	UG10327, MCX, MCX E31x
Abstract	Hardware design guide for MCX E31x MCU, covering power, decoupling, crystal, and Ethernet



MCX E31x Hardware Design Guide

1 Introduction

The MCX E31x microcontroller expands the Arm Cortex MCU portfolio within the MCX family with higher memory options and along side a richer peripheral set, extending capability into various industry applications.

The MCX E31x series devices are well suited to a wide range of applications in electrical harsh environments. This enhancement extends its capabilities to various industry applications, particularly in electrically harsh environments. The MCX E31x series devices are optimized for cost-sensitive applications with low pin-count options.

The purpose of this user guide is to describe possible hardware considerations using the MCX E31x microcontroller in the industry. It covers the most important topics such as the power considerations, bulk/ bypass and decoupling capacitors required, reset, crystal, Ethernet, and QSPI configurations. This document also provides PCB Layout recommendations.

2 Power system

The following sections describe different options for power supply configurations, and cover considerations for proper connection of supply and ground pins.

2.1 MCX E31x power domains and configurations

The MCX E31B microcontroller features two flexible and externally supplied power domains: VDD_HV_A, VREFH, and VDD_HV_B. These can be powered at the same or different voltage levels depending on application requirements. Also, it includes a V15 domain to +1.5 V that can be supplied using an external NPN ballast transistor. In contrast, the MCX E315, MCX E316, and MCX E317 variants have a single power domain, VDD_HV_A. This VDD_HV_A reference is the voltage domain for their IOs pins.


<u>Table 1</u> shows all positive power pins and domains that must be supplied externally along with internal MCU references.

Table 1. Power supply pins and domains


MCU	Package	Power supply pins and domains							
		VDD_HV_A	VREFH	VDD_HV_B	V15	V25	V11		
		+3.3 V or +5.0 V	≤ VDD_HV_A	+3.3 V or +5.0 V	+1.5 V	+2.5 V	+1.1 V		
MCX E31B	172 HDQFP	Domain and Ref. voltage for I/O pins	ADC high reference voltage	Domain and Ref. voltage for I/O pins	Power supply input	Internal MCU reference	Internal MCU reference		
MCX E317 MCX E316 MCX E315	48 LQFP 100 HDQFP 172 HDQFP	Domain and Ref. voltage for I/O pins	ADC high reference voltage	NA	NA	Internal MCU reference	Internal MCU reference		

This section covers only an overview of the voltage domains for the different interfaces and I/Os in the MCU. Refer to the latest version of the device *Data sheet* and *Reference Manual* for more details.


MCX E31x Hardware Design Guide

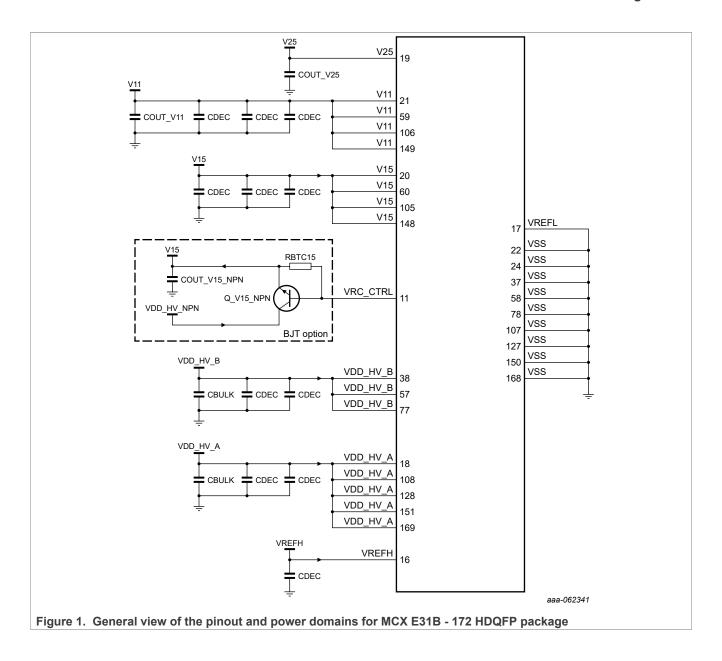

MCX E31x Hardware Design Guide

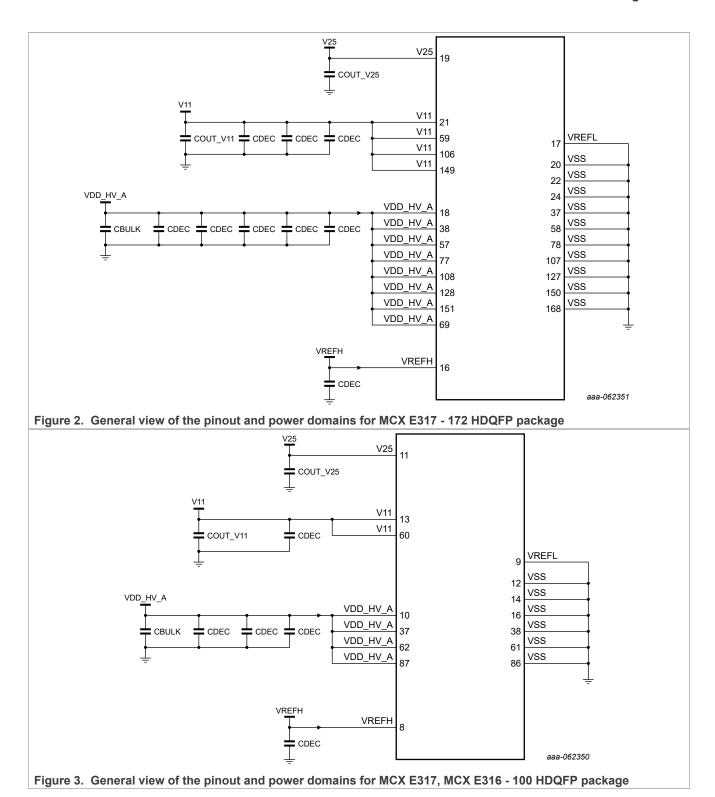

MCX E31x Hardware Design Guide

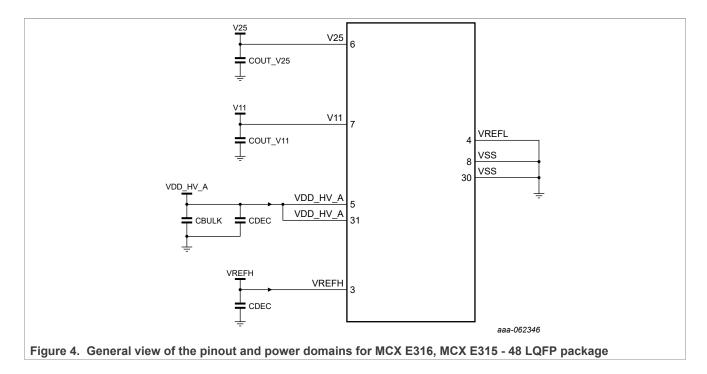

2.2 VDD_HV_A - main I/O and analog supply voltage

VDD_HV_A is the main I/O and analog supply voltage in the MCX E31x MCU. The VDD_HV_A domain must be connected to an external power supply of +3.3 V or +5.0 V. An off-chip local Bulk/bypass and decoupling capacitors between the VDD_HV_A pins and the VSS reference are required.

Table 2. VDD_HV_A - main I/O and analog supply pins

MCU pin			J package - pin n	umber		Comments
name	operating voltage	MCX E315/316 48 LQFP	MCX E315/316/317 100 HDQFP	MCX E31B 172 HDQFP	MCX E317 172 HDQFP	
VDD_HV_A	+3.3 V	5	10	18	18	All VDD_HV_A pins
	or +5.0 V	31	62	108	108	must be shorted and connected externally
	+3.0 V	-	87	128	128	to a common reference
		-	37	151	151	on the PCB. Use a decoupling capacitor
		- 37 151 151 decoupling for each s Add a local capacitor VDD_HV_increase to and decoupling to this voltage.	for each supply pin. Add a local bulk/bypass capacitor just for the VDD_HV_A domain, to increase the robustness and decoupling effect on this voltage reference of the MCU.			

2.3 VREFH - ADC high reference voltage

VREFH is the ADC high reference voltage. An off-chip decoupling capacitor between the VREFH pin and the VSS/VREFL reference is required.

UG10327

All information provided in this document is subject to legal disclaimers.

© 2025 NXP B.V. All rights reserved.

MCX E31x Hardware Design Guide

The VREFH is the ADC high reference voltage in the MCX E31x MCU. The VREFH pin must be connected to an external power supply or a reference voltage ≤ VDD_HV_A. An off-chip local decoupling capacitor between the VREFH pin and the VSS/VREFL reference is required.

Table 3. VREFH - ADC high reference voltage

MCU pin	Normal operating	MCX E31x MCU	Comments			
name	voltage	MCX E315/316 48 LQFP	MCX E315/316/317 100 HDQFP	MCX E31B 172 HDQFP	MCX E317 172 HDQFP	
VREFH	≤VDD_HV_A	3	8	16	16	A decoupling capacitor must be used on the supply pin.
VREFL	GND	4	9	17	17	

2.4 VDD_HV_B - secondary I/O supply voltage

The VDD_HV_B is the secondary I/O supply voltage in some versions of the MCX E31x MCU family. The VDD_HV_B domain must be connected to an external power supply of +3.3 V or +5.0 V. An off-chip local Bulk/ bypass and decoupling capacitors between the VDD_HV_B pins and the VSS reference are required.

Table 4. VDD_HV_B - secondary I/O supply voltage

MCU pin	Normal	MCX E31x MCL	MCX E31x MCU package - pin number						
name	operating voltage	MCX E315/316 48 LQFP	MCX E315/316/317 100 HDQFP	MCX E31B 172 HDQFP	MCX E317 172 HDQFP				
VDD_HV_B	+3.3 V	-	-	38	-	All VDD_HV_B pins			
	or +5.0 V	-	-	57	-	must be shorted and connected externally			
	10.0 V	-	-	77	-	to a common reference on the PCB. Use a decoupling capacitor for each supply pin. Add a local bulk/bypass capacitor for the VDD_HV_B domain to increase the robustness and decoupling effect on this voltage reference of the MCU.			

2.5 V11 - core logic voltage supply (+1.1 V)

V11 is the internally generated core logic voltage supply. An off-chip Bulk/bypass, decoupling and filter capacitors between the V11 pins and the VSS reference is highly recommended. This reference voltage must not be used or connected to other interfaces in the application.

MCX E31x Hardware Design Guide

Table 5. V11 – Core logic voltage supply (+1.1 V)

MCU pin name	Normal operating voltage	MCX E31x M	Comments			
		MCX E315/316 48 LQFP	MCX E315/316/317 100 HDQFP	MCX E31B 172 HDQFP	MCX E317 172 HDQFP	
V11	+1.1 V	7	13	21	21	All V11 pins must
	Internal voltage reference	-	60	59	59	be shorted and connected externally
	reference	-	-	106	106	together to a
		-	-	149	149	common reference on the PCB. Use a decoupling capacitor for each supply pin. Add a local bulk/ bypass capacitor for the V11 domain to increase the robustness and decoupling effect on this voltage reference of the MCU.

2.6 V25 - flash memory supply (+2.5 V)

V25 is the internally generated flash memory supply. An off-chip filtering and decoupling capacitor between the V25 pin and the VSS reference is required. This reference voltage must not be used or connected to other interfaces in the application.

Table 6. V25 - Flash memory supply (+2.5 V)

MCU pin name	Normal operating voltage	MCX E31x MC	Comments			
		MCX E315/316 48 LQFP		MCX E31B 172 HDQFP	MCX E317 172 HDQFP	
V25	+2.5 V Internal voltage reference	6	11	19	19	This internal reference voltage must not be used or connected to other interfaces in the application.

2.7 V15 - high-current logic supply voltage (+1.5 V)

V15 is the high-current logic supply voltage for some MCU versions of the MCX E31x family. The MCX E31x MCU provides the option to supply the voltage reference either using an external NPN ballast transistor and a stability ceramic capacitor or supplying externally by an SBC to +1.5 V. An off-chip bulk/bypass capacitor and a decoupling capacitor between each V15 pin and the VSS reference are required for both configurations. This MCU reference voltage must not be used or connected to other interfaces in the application.

MCX E31x Hardware Design Guide

Table 7. V15 - high current logic supply voltage

MCU pin	Normal	MCX E31x MCU	package - pin nu	mber		Comments			
name	operating voltage	MCX E315/316 48 LQFP	MCX E315/316/317 100 HDQFP	MCX E31B 172 HDQFP	MCX E317 172 HDQFP				
V15	+1.5 V	-	-	20	-	All V15 pins			
	High-current logic supply voltage	-	-	60	-	must be shorted and connected			
	supply voltage	supply voltage	supply voltage	Supply Voltage	-	-	105	-	externally to a common reference
		-	-	148	-	on the PCB. Use a decoupling capacitor for each supply pin. Add a local bulk/ bypass capacitor for the V15 domain to increase the robustness and decoupling effect on this voltage reference of the MCU.			

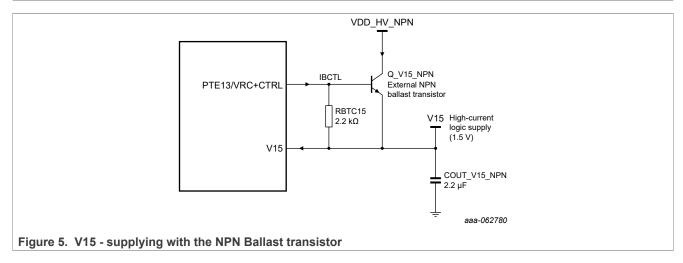


Table 8. V15 - component description and values for the external NPN Ballast transistor option

Symbol	Characteristic	Value						
Q_V15_NPN	NPN Ballast transistor	-						
RBCT15	Metal film resistor	2.2 kΩ						
COUT_V15	Stability capacitor. X7R ceramic or tantalum	2.2 µF						
CDEC ^[1]	Decoupling capacitor	100 nF – 220 nF						
1.								

^[1] A decoupling capacitor can be used per each supply pin and a local Bulk/bypass capacitor just for the V15 domain, to increase the robustness and decoupling effect on this voltage reference of the MCU.

MCX E31x Hardware Design Guide

2.8 VSS and VREFL - Ground and ADC reference low

All VSS pins and VREFL pin of the MCU must be externally connected in a continuous and single solid GND plane.


Table 9. VSS pins - MCU Ground reference

MCU pin	Normal	MCX E31x MCU	package - pin nu	mber		Comments
name operating voltage		MCX E315/316 48 LQFP	MCX E315/316/317 100 HDQFP	MCX E31B 172 HDQFP	MCX E317 172 HDQFP	
VSS	0 V-GND	8	12	22	20	All VSSx pins
		30	14	24	22	and the VREFL pin of the MCU
		-	16	37	24	must be externally
		-	38	58	37	connected in a continuous and
		-	61	78	58	single solid GND
		-	86	107	78	plane as mandatory.
		-	-	127	107	
		-	-	150	127	
		-	-	168	150	
		-	-	-	168	
VREF	VSS	4	9	17	17	

2.9 Bulk and decoupling capacitors

The effectiveness of the bulk/bypass and the decoupling capacitors depends on the optimal placement and connection type. The bulk capacitor acts as a local power supply for the power pin. It should be placed near the decoupling capacitors and as close as possible to the assigned reference voltage pin. Decoupling capacitors make the current loop between supply, MCU, and ground reference as short as possible for high-frequency transients and noise. Therefore, each decoupling capacitor should be placed as close as possible to each of its respective power supply pin. The ground side of the decoupling capacitor should have a via to the pad, which goes directly down to the ground plane.

MCX E31x Hardware Design Guide

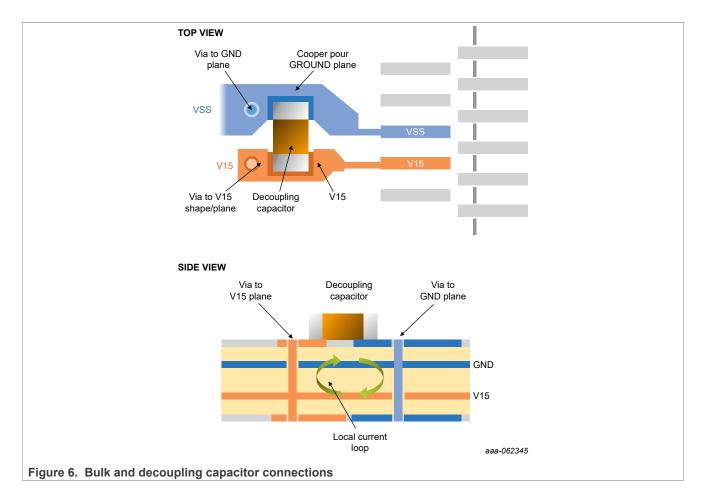

2.10 Power considerations

The MCX E31x MCU has great versatility in its power supply because in some models (MCX E31B) it integrates three external power domains (VDD_HV_A, VDD_HV_B, and V15), and can generate other voltages using some special pins such as VRC_CTRL (only available in some models). These special pins can be activated or deactivated. However, Domain A and Domain B cannot be deactivated by any Software command.


If power to Domain B is removed externally, the microprocessor resets due to built-in voltage sensors and indicator flags that detect power issues, protecting the microcontroller. However, if power to Domain A is removed externally, the entire MCX E31x shuts down.

2.10.1 MCU power supply ramp rate

During power-on of the MCU, the power supply must assure a ramp-rate within this range from VDD_OFF (= 0.1 V) to the voltage operating level of VDD_HV_A, VDD_HV_B, and V15. The outcome of violating the specification causes unexpected behavior, stuck operation or damage in the MCU.

Note: For detail on the maximum and minimum limit of MCU supply ramp rate, refer to the MCX E31x device data sheet.

MCX E31x Hardware Design Guide

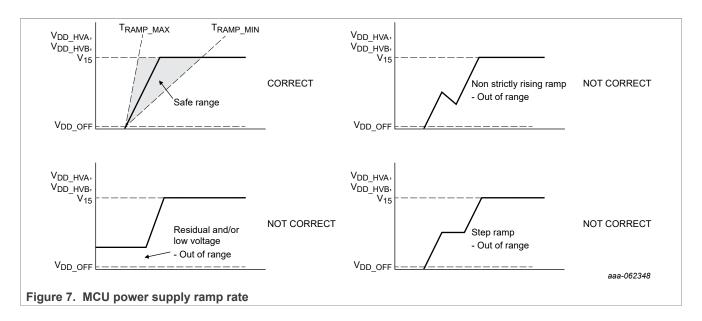

2.11 Pinout differences between MCX E31B - 172 HDQFP and MCX E317 - 172 HDQFP

Table 10 describes the pinout differences between MCX E31B - 172 HDQFP and MCX E317 - 172 HDQFP.

Table 10. Pinout differences between MCX E31B - 172 HDQFP and MCX E317 - 172 HDQFP

172	MCX E317	,		MCX E31B		Topology recommended for a drop-in
HDQFP MCU pin number	Pin name	Pin function	I/O power domain	Pin name	Pin function	replacement between an MCX E317 and an MCX E31B on a 172 HDQFP package
11	PTE13	Ю	VDD_HV_ A	PTE13	VRC_ CTRL - PMC voltage regulator control output [4]	NPN ballast RSC PTE13 aaa-062347 See [1], [2], [3], [4]
20	VSS	Supply GND	-	V15	+1.5 V - High- current logic supply voltage	20 RDC CDEC eaa-062342 See [1], [2], [3], [4]
60	РТВ30	Ю	VDD_HV_ A	V15	+1.5 V - High- current logic supply voltage	RDC V15 RSC PTB30 aaa-062353

MCX E31x Hardware Design Guide

Table 10. Pinout differences between MCX E31B - 172 HDQFP and MCX E317 - 172 HDQFP...continued

172	MCX E317	,		MCX E31B		Topology recommended for a drop-in
HDQFP MCU pin number	Pin name	Pin function	I/O power domain	Pin name	Pin function	replacement between an MCX E317 and an MCX E31B on a 172 HDQFP package
						See [1], [2], [3], [4]
105	PTD18	Ю	VDD_HV_ A	V15	+1.5 V - High- current logic supply voltage	105 RDC CDEC RSC PTD18 aaa-062352 See [1], [2], [3], [4]
148	PTE19	Ю	VDD_HV_ A	V15	+1.5 V - High- current logic supply voltage	148 RDC CDEC RSC PTE19 aaa-062344 See [1], [2], [3], [4]
38	VDD_ HV_A	VDD_ HV_A - main I/ O and analog supply voltage	-	VDD_HV_ B	VDD_ HV_B - secondary I/O supply voltage	VDD_HV_B VDD_HV_A RDC RSC RSC aaa-062343 See [1], [2], [3], [5], [6]
57	VDD_ HV_A	VDD_ HV_A - main I/ O and analog supply voltage	-	VDD_HV_ B	VDD_ HV_B - secondary I/O supply voltage	VDD_HV_B VDD_HV_A RDC RDC RSC aaa-062349 See [1], [2], [3], [5], [6]
77	VDD_ HV_A	VDD_ HV_A - main I/ O and analog supply voltage	-	VDD_HV_ B	VDD_ HV_B - secondary I/O supply voltage	VDD_HV_B VDD_HV_A RDC RSC GDEC RSC aaa-062357 See [1], [2], [3], [5], [6]

 $R_{DC} = R_{SC} = 0 \Omega$.

 R_{DC} must be used just for MCX E31B and R_{SC} should be removed.

R_{SC} must be used just for MCX E317, and R_{DC} should be removed.

^[3] [4] The V15 reference for the MCX E31B should have all considerations mentioned in <u>Section 2.7</u>.

The VDD_HV_A reference for the MCX E317 should have all considerations mentioned in Section 2.2. The VDD_HV_B reference for the MCX E31B should have all considerations mentioned in Section 2.4.

MCX E31x Hardware Design Guide

3 Clock circuitry

The MCX E31x MCU has the following clock sources:

- 8 MHz 40 MHz fast external oscillator (FXOSC)
- 48 MHz fast internal reference clock oscillator (FIRC)
- 32 kHz low-power oscillator (SIRC)
- 32 kHz slow external oscillator (SXOSC)
- Up to 320 MHz system phased lock loop (SPLL)

FIRC and SIRC are internal and do not have to be considered from the hardware design perspective. The external oscillator works with a range from 8 MHz to 40 MHz. It provides an output clock that can be provided to the PLL or used as a clock source for some peripherals. When using the external oscillator as the input source for the PLL, the frequency range of the external oscillator should be 8 MHz to 40 MHz.

3.1 EXTAL and XTAL pins

These pins provide the interface for a crystal to control the internal clock generator circuitry. EXTAL is the input to the crystal oscillator amplifier. XTAL is the output of the crystal oscillator amplifier. The Pierce oscillator provides a robust, low-noise, and low-power external clock source. It is designed for optimal startup margin with typical crystal oscillators. The MCX E31x MCU supports crystals or resonators ranging from 8 MHz to 40 MHz. The input capacitance of the EXTAL and XTAL pins is 7 pF.

Table 11. EXTAL and XTAL pins

- 1	operating voltage	MCX E31x MCU	Comments			
name		MCX E315/316 48 LQFP	MCX E315/316/317 100 HDQFP	MCX E31B 172 HDQFP	MCX E317 172 HDQFP	
XTAL	External crystal output	10	17	25	25	
EXTAL	External crystal input	9	15	23	23	

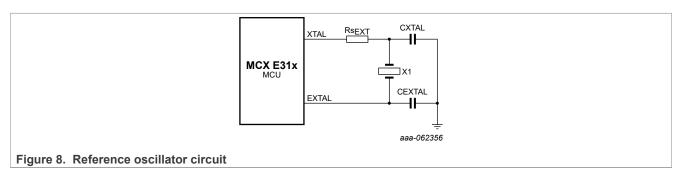


Table 12. Components of the oscillator circuit

Table 121 Compensate of the Commeter of Call				
Symbol	escription			
RsEXT	Series resistor for current limitation			
X1	Quartz crystal / ceramic resonator			
CXTAL	External load capacitor on XTAL pin			
CEXTAL	External load capacitor on EXTAL pin			

UG10327

MCX E31x Hardware Design Guide

Table 12. Components of the oscillator circuit...continued

Symbol	Description				
The Rs and load canacitors values depend on the specifications of the crystal and on the hoard canacitance. It is					

recommended to develop evaluation and characterization of the crystal on the PCB in collaboration with the part manufacturer.

4 Debug and programming interface

This section explains best practices for debugging and programming the MCX E31x MCU, including reset mechanisms, external reset pin considerations, and JTAG/TRACE connectivity.

4.1 RESET system

Resetting the MCU provides a way to start processing from a known set of initial conditions. System reset begins with the on-chip regulator in full regulation and system clocking generation from an internal reference.

4.2 External pin RESET

For all reset sources, the RESET_B pin is driven low by the MCU for at least 128 bus clock cycles and until flash memory initialization has completed. After flash memory initialization has completed, the RESET_B pin is released and the internal chip reset deasserts. Keeping the RESET_B pin asserted externally delays the negation of the internal chip reset. The RESET pin is the same as the standard SIUL2_GPIO/eMIOS_GPIO. It can operate as a pseudo-open-drain output because there is also a PMOS device in the output stage.

The reset pin, similar to some other GPIO has a weak internal pullup. If the environment and the customer application are noisy, an external pullup resistor to VDD_HV_A must be added directly to the reset pin to avoid a sporadic or unintended reset occurs. Refer to the device data sheet for the levels of voltage and current allowed in the pin. A capacitor in the reset line is not directly required for the MCU. However, an external capacitor can be added between the RESET pin and the ground for additional ESD protection. If used, this capacitor should be placed as close as possible to the debug interface or connector. The values of the pullup resistor and the capacitor must be selected according to the design requirements of the application. Refer to the device data sheet for the minimum RESET pulse value that can be detected for the MCU.

4.3 JTAG and TRACE interface

A number of commonly used debug connectors are shown here. Most of the Arm development tools use one of these pins. When developing your Arm circuit board, it is recommended to use a standard debug signal arrangement to make connection to the debugger easier:

Table 13. JTAG signal description

_	Description	MCU pin	MCX E31x MCU package - pin number				Recommend	
name		name		MCX E315/316/31 100 HDQFP	MCX E31B 172 HDQFP	MCX E317 172 HDQFP		domain
JTAG_TDO	JTAG test data output	PTA10	44	92	161	161	Pullup	VDD_HV_A
JTAG_TDI	JTAG test data input	PTC5	45	95	165	165	Pullup	
JTAG_TCK/ SWD_CLK	Clock into the core	PTC4	46	96	166	166	Pulldown	

MCX E31x Hardware Design Guide

Table 13. JTAG signal description...continued

Signal Description MCU pin			MCX E31x MCU package - pin number				Recommend	
name		name	MCX E315/316 48 LQFP	MCX E315/316/317 100 HDQFP		MCX E317 172 HDQFP		domain
JTAG_TMS/ SWD_DIO	JTAG test mode select	PTA4	48	98	170	170	Pullup	
RESET	Reset MCU	PTA5	47	97	167	167	Pullup	

External pullup/down resistors for the JTAG signals can be added to increase debugger connection robustness.

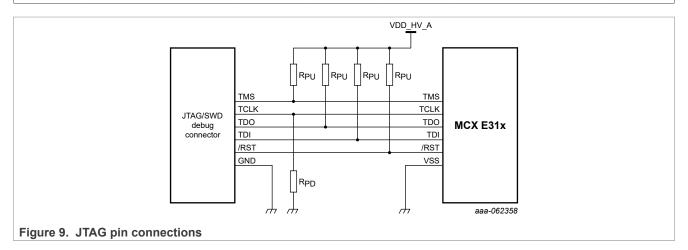


Table 14. JTAG connector - Component description

Symbol	Parameter	Typ value range	Units
R _{PU}	Pullup resistor	4.7 k-10 k	Ω
R _{PD}	Pulldown resistor	4.7 k-10 k	Ω

5 Communication modules

When in an application, different voltage levels in the MCU domains are used (for example VDD_HV_A = +5.0 V and VDD_HV_B = +3.3 V), ensure that the following communication interfaces are configured to use the same voltage domain (VDD_HV_A or VDD_HV_B).

- FlexCAN
- LPUART
- LPI2C
- LPSPI
- QSPI
- Ethernet MAC
- SAI

Also, verify that the data lines are within the voltage range allowed for that communication. For example, VDD_HV_B = +3.3 V in the case of Ethernet MAC, SAI, and QSPI.

A cross-combination of voltage domains for communication interfaces is not allowed (for example, the TX data line with VDD_HV_A and the RX data line with VDD_HV_B).


UG10327

MCX E31x Hardware Design Guide

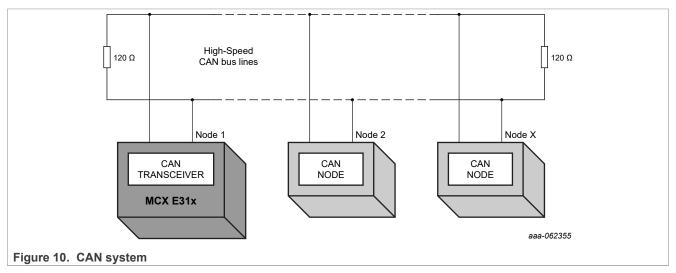5.1 CAN interface

The physical layer characteristics for CAN are specified in ISO-11898-2. This standard specifies the use of cable comprising parallel wires with an impedance of nominally 120 Ω (95 Ω as minimum and 140 Ω as maximum). The use of shielded twisted pair cables is necessary for electromagnetic compatibility (EMC) reasons, although ISO-11898-2 also allows for unshielded cable. A maximum line length of 40 meters is specified for CAN at a data rate of 1 Mb. However, at lower data rates, potentially much longer lines are possible. ISO-11898-2 specifies a line topology, with individual nodes connected using short stubs.

Though not exclusively intended for automotive applications, the CAN protocol is designed to meet the specific requirements of a vehicle serial data bus: real-time processing, reliable operation in the EMI environment of a vehicle, cost-effectiveness, and required bandwidth. Each CAN station is connected physically to the CAN bus lines through a transceiver device. The transceiver can drive the large current needed for the CAN bus and has current protection against defective CAN or defective stations. A typical CAN system with an MCX E31x microcontroller is shown in Figure 10.



The CAN module is a full implementation of the CAN protocol specification, the CAN with flexible data rate (CAN FD) protocol and the CAN 2.0 version B protocol, which supports both standard and extended message frames and long payloads up to 64 bytes transferred at faster rates up to 8 Mbit/s. The message buffers are stored in an embedded RAM dedicated to the CAN module. See the chip configuration details in the Device Reference Manual for the number of message buffers configured in the chip.


Like most other CAN physical transceivers, the CANH, CANL, and SPLIT pins are available for the designer to terminate bus depending on the application. <u>Figure 11</u> shows examples of the CAN node terminations.

Note:

When operating with different voltage levels in MCU domains (for example, VDD_HV_A = +5.0 V and VDD_HV_B = +3.3 V), ensure that the CANx_TX/RX data lines meet the following requirements:

- 1. The CANx_TX/RX data lines must operate within the same voltage domain (VDD_HV_A or VDD_HV_B).
- 2. The data lines must be within the voltage range allowed for communication with the CAN Physical layer.

MCX E31x Hardware Design Guide

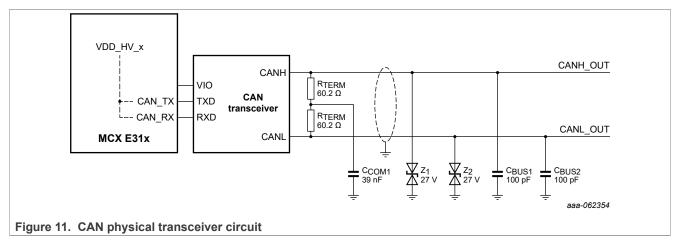

CAN components data

Table 15. CAN components

Reference	Description
CBUS1 and CBUS2	The Capacitors CBUS1 and CBUS2 are not required. They may be added for EMC reasons, in which case the maximum capacitance from either bus wire to ground must not exceed 300 pF total. If Zener stacks are also needed, the parasitic capacitance of the Zener stacks must also be included in the total capacitance budget.
Z1 and Z2	The Zener stacks Z1 and Z2 could be required to satisfy Automotive EMC requirements (ESD in particular). These devices should be placed close to the connector.
RTERM1, RTERM2, and CCOM1	Depending on the position of the node within the CAN network it might need a specific termination. RTERM1, RTERM2, and CCOM1 must be that they assist in having an overall cable impedance. On a bus implementation of a CAN network only the two nodes on the two ends of the bus have terminator resistors. The nodes not placed on the end of the CAN bus do not have termination. A thorough analysis is required to maintain this requirement of the CAN networks. The SPLIT pin on the transceiver is optional and the designer might choose not to use it. This pin helps stabilize the recessive state of the CAN bus and can be enabled or disabled by software when required.
LBUS1–Common mode choke	A common mode choke on the CANH and CANL lines can help reduce coupled electromagnetic interference and needed to satisfy Automotive EMC requirements. This choke, together with transient suppressors on the transceiver pins, can greatly reduce coupled electromagnetic compatibility noise, and high frequency transients. LBUS1 is not required.

CAN termination:

In a transmission line, there are two current paths, one to carry the currents from the driver to the receiver and another to provide the return path back to the driver. The CAN transmission lines are complex because there are two signals that are sharing a common termination and a ground return path. For reliable CAN communications, it is essential that the reflections in the transmission line be kept as small as possible. This can only be done by proper cable termination.

Reflections happen quickly during and just after signal transitions. On a long line, the reflections are more likely to continue long enough to cause the receiver to misread logic levels. On short lines, the reflections occur sooner and have no effect on the received logic levels.

MCX E31x Hardware Design Guide


5.2 Ethernet MAC interface

The MII/RMII interface signal can be directly routed to the MAC-NET interface. However, series termination resistors may be considered on RXCLK, TXCLK, and all RX/TX signals for EMI suppression. These resistors should be placed within 100 mils of the Ethernet physical interface and routed to an uninterrupted reference plane. Series termination resistors with value between 33 Ω and 50 Ω are commonly recommended to improve electromagnetic interference (EMI) performance.

Although RMII and MII are synchronous bus architectures, various factors limit signal trace lengths. With a longer trace, the signal becomes more attenuated at the destination and therefore more susceptible to noise interference. Longer traces also act as antennas, and if run on the surface layer, can increase EMI radiation. If a long trace is running near and adjacent to a noisy signal, the unwanted signals could be coupled in as crosstalk. It is recommended to keep the signal trace lengths as short as possible. Ideally, keep the traces under 6 inches. Trace length matching to within 2.0 inches on the MII or RMII bus is also recommended. Significant differences in the trace lengths can cause data timing issues. Minimize the use of vias throughout the design. Vias add capacitance to signal traces. As with any high-speed data signal, good design practices dictate that impedance should be maintained and stubs should be avoided throughout the entire data path.


Because the TX and RX data signals are triggered by the rising edge of the clock, communication in MII and RMII is synchronous. Therefore, the length of the EMAC data lines and the clock line between the K3 microcontroller and the PHY must be matched. The allowed deviation in length matching depends on the rise/fall time for digital signals between these two elements, although it is recommended that any deviation be less than 10 mm as MII and RMII.

MII signaling: Figure 12 shows the PHY-MAC and MAC-MAC connections in an MII interface. Data is exchanged via 4-bit wide data nibbles TXD[3:0] and RXD[3:0]. Data transmission is synchronous with the transmit (TX_CLK) and receive (RX_CLK) clocks. For the PHY-MAC interface, both clock signals are provided by the PHY and are typically derived from an external crystal running at a nominal 25 MHz or from the CLK_OUT signal on the switch. When the Ethernet Switch is configured for MAC-MAC communication, the switch provides the clocks and acts like a PHY.

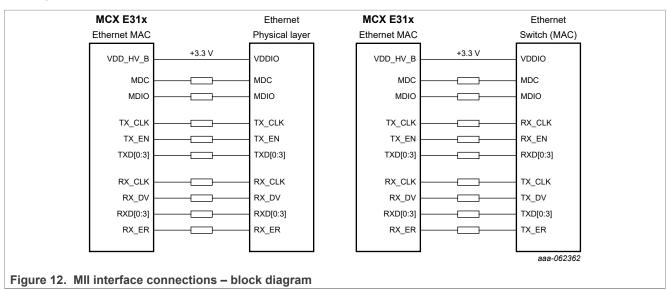

RMII signaling: RMII data is exchanged via 2-bit data signals TXD[1:0] and RXD[1:0] as shown in <u>Figure 13</u>. Transmit and receive signals are synchronous with the shared reference clock, REF_CLK.

MCX E31x Hardware Design Guide

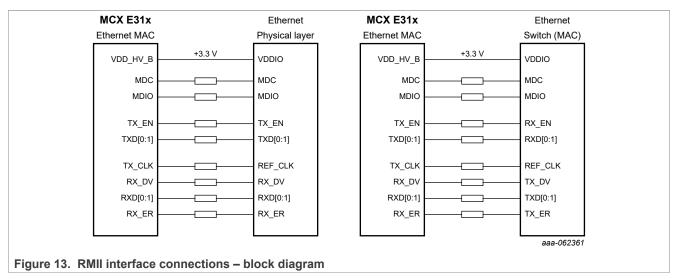


Noto

All signals of the Ethernet MAC module of the MCX E31x microcontroller are in the VDD_HV_B domain. A method for voltage level translation is not required in the Ethernet Physical layer or MAC interface since the VDD_HV_B domain should be connected to +3.3 V.

6 Quad serial peripheral interface

The MCX E31x MCU has one instance of QuadSPI. The quad serial peripheral interface (QuadSPI) block acts as an interface to an external serial flash device. It supports SDR mode up to 4 bidirectional data lines respectively. The QuadSPI supports an A-side. The following external memory option can be supported:

Single Quad Flash on the A-side

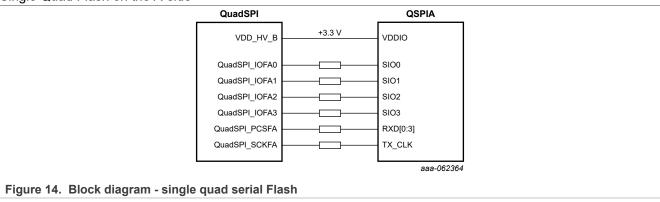

Note: All signals of the QSPI module of the MCX E31x microcontroller are in the VDD_HV_B domain. A method for voltage level translation is not required in the QSPI memory interface since the VDD_HV_B domain should be connected to +3.3 V.

Table 16. QSPI signal description

Signal name	MCU pin name	MCX E31x MCU		I/O power		
		70 LQ11		MCX E31B 172 HDQFP	MCX E317	domain
QuadSPI_PCSFA	PTC3	-	-	49	-	VDD_HV_B

UG10327

All information provided in this document is subject to legal disclaimers

© 2025 NXP B.V. All rights reserved.


MCX E31x Hardware Design Guide

Table 16. QSPI signal description...continued

Signal name	MCU pin name	MCX E31x MCU	I/O power			
		MCX E315/316 48 LQFP	MCX E315/316/317 100 HDQFP	MCX E31B 172 HDQFP	MCX E317 172 HDQFP	domain
QuadSPI_IOFA3	PTC2	-	-	50	-	VDD_HV_B
QuadSPI_IOFA2	PTD12	-	-	54	-	VDD_HV_B
QuadSPI_IOFA1	PTD7	-	-	51	-	VDD_HV_B
QuadSPI_IOFA0	PTD11	-	-	55	-	VDD_HV_B
QuadSPI_SCKFA	PTD10	-	-	56	-	VDD_HV_B

Data and clock signal termination: Clock generation and distribution become more difficult as the speed and performance of microprocessors increase to higher limits. Controlled and precise clocking distribution techniques are needed to maintain a synchronous system. Clock signal quality and skew are the two major problems with distributing clock signals. With higher frequencies, and the associated fast edge rates, long traces behave like transmission lines. Ring back, overshoot, and undershoot occur as a result of poor termination of transmission lines. They contribute to bad signal quality, false switching, and they can cause damage in extreme cases.

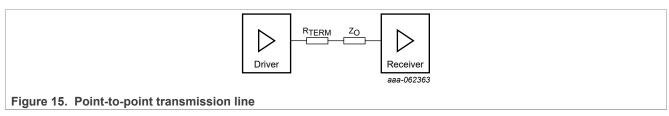Given the effective output driver strength of 22 Ω to 33 Ω and the transmission line characteristic impedance of 50 Ω , you should add the termination resistor close to the output driver, to minimize the reflection as shown in Figure 15.



Data signal routing: To keep the correct timing for the data transfer from the microcontroller to the IC memory, the PCB data traces should be the same length and time delay as the clock trace from the microcontroller to the IC memory. Data signals should be routed with controlled impedance traces to reduce signal reflections. Avoid routing traces with 90 ° angle corners. The recommendation is to cut the corner and smooth the trace when a trace route must change direction. To improve the signal integrity further, avoid using multiple signal layers for data signal routing. All signal traces should have a continuous and solid GND reference plane.

Clock signal routing: In high-speed synchronous data transfer, good signal integrity in a PCB design is of critical importance, especially for the clock signals, SCLK and DQS. When routing the clock signal, special care should be taken. The following practices are recommended.

- Run the clock signal at least 3W of the trace width away from all other signal traces. This helps keep the clock signal clean from crosstalk noise.
- Use as few via(s) as possible for the whole signal path, each signal via should have a ground transition
 via next to them; without this, the signal routing could have an impedance change and to cause a signal
 reflection.
- All signal traces should go with a solid GND reference plane.
- · Run the clock trace as straight as possible and avoid using serpentine routing.
- Keep a continuous ground in the next layer as a reference plane.
- Keep as much space between high-speed routing (differential pairs, clock routing, and so on) and other
 routing. The general principle here is that by spacing out traces at three times their line width, measured
 center to center, 70 % of their electrical field can be stopped from mutual interference.

UG10327

MCX E31x Hardware Design Guide

7 Unused pins

<u>Table 17</u> describes the options and configurations for the unused pins and the considerations for other modules and sections of the MCU.

Table 17. Unused pins configuration

Module	Pin name	Function	Recommendation			
GPIO	PTx	ENETx	The unused GPIO should be left unconnected or externally connected			
		FTMx	to VSS/GND reference.			
		FlexIOx				
		CANx				
		LPUARTx				
		LPI2Cx				
		ADCx				
		СМРх				
		Others				
External Clock	XTAL	XTAL	The pins with the XTAL and EXTAL functions must be left			
	EXTAL	EXTAL	unconnected if not in use.			
JTAG	PTA4	JTAG_TMS	Since these pins have either internal weak pullups (TDI, TDO			
	PTA10	JTAG_TDO	and TMS) or pulldown (TCK) it is ok to add external pull resistors in parallel to the internal ones to increase debugger connection robustness.			
	PTC5	JTAG_TDI				
	PTC4	JTAG_TCK				
RESET	PTA5	PTA5/TCLK1/ RESET_b	The reset pin cannot be left unconnected. It must be pulled up to VDD_HV_A with an external resistor directly to the RESET pin. Refer to the chapter of RESET system.			
Power	VDD_HV_A	Main I/O and Analog Supply Voltage	No VDD_HV_A, VREFH, and VDD_HV_B power pin should be left unconnected or unpowered. All power pins must be shorted together			
	VDD_HV_B	Secondary I/O Supply Voltage	externally on their voltage domain. Appropriate bulk/bypass and decoupling capacitors should be used.			
	VREFH	ADC High Reference Voltage				
	V15	High-current logic supply voltage (+1.5 V)	No V15 power pin should be left unconnected or unpowered. All V15 power pins must be shorted together externally on their voltage domain. Appropriate bulk/bypass and decoupling capacitors should be used to filter noise on the supply. Refer to the chapter in this document.			
	V11	Core logic voltage supply (+1.1 V)	No V11 power pin should be left unconnected. All V11 power pins must be shorted together externally on their voltage domain. Appropriate bulk/bypass and decoupling capacitors should be used to filter noise on the supply. Refer to the chapter in this document. The V11 domain must not be used or connected to other interfaces in the application.			
	V25	Flash memory supply (+2.5 V)	The V25 power pin should not be left unconnected; the decoupling capacitor should be used to filter noise on the supply. Refer to the chapter in this document. The V25 domain must not be used or connected to other interfaces in the application.			

MCX E31x Hardware Design Guide

Table 17. Unused pins configuration...continued

Module	Pin name	Function	Recommendation
Ground	VSSx		No VSSx/VREFL pin should be left unconnected. All VSSx/VSS_
	VREFL	ADC Low Reference Voltage	DCDC and VREFL must be shorted together externally to GND.

8 References

For more detail on MCX E31x devices, refer to the following documents.

- MCXE315/316/317/31B Robust 5V Arm Cortex M7 MCU, SIL2 compliant (MCXEP172M160FB0)
- MCXE31x Reference Manual (MCXE31XRM)

9 Acronyms

Table 18. Acronyms

Term	Description	
EMAC	Ethernet media access controller	
EMC	Electromagnetic compatibility	
ESD	Electrostatic discharge	
ESD	Electrostatic discharge	
FIRC	Fast internal reference clock	
FlexCAN	Flexible controller area network interface	
GPIO	General-purpose input/output	
HDQFP	High-density quad flat package	
JTAG	Joint test action group	
LPI2C	Low-power inter-integrated circuit	
LPSPI	Low-power serial peripheral interface	
LPUART	Low-power universal asynchronous receiver/transmitter	
MAC	Media access controller	
MII	Media-independent interface	
NPN	Negative-positive-negative	
РСВ	Printed-circuit board	
РСВ	Printed-circuit board	
PMOS	P-channel metal-oxide semiconductor	
QSPI	Quad serial peripheral interface	
RMII	Reduced media-independent interface	
SAI	Serial audio interface	
SIRC	Slow internal reference clock	

MCX E31x Hardware Design Guide

10 Revision history

Table 19 summarizes revisions to this document.

Table 19. Revision history

Document ID	Release date	Description
UG10327 v.1.0	9 October 2025	Initial public release

MCX E31x Hardware Design Guide

Legal information

Definitions

Draft — A draft status on a document indicates that the content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included in a draft version of a document and shall have no liability for the consequences of use of such information.

Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. NXP Semiconductors takes no responsibility for the content in this document if provided by an information source outside of NXP Semiconductors.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors and its suppliers accept no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Terms and conditions of commercial sale — NXP Semiconductors products are sold subject to the general terms and conditions of commercial sale, as published at https://www.nxp.com/profile/terms, unless otherwise agreed in a valid written individual agreement. In case an individual agreement is concluded only the terms and conditions of the respective agreement shall apply. NXP Semiconductors hereby expressly objects to applying the customer's general terms and conditions with regard to the purchase of NXP Semiconductors products by customer.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

Suitability for use in non-automotive qualified products — Unless this document expressly states that this specific NXP Semiconductors product is automotive qualified, the product is not suitable for automotive use. It is neither qualified nor tested in accordance with automotive testing or application requirements. NXP Semiconductors accepts no liability for inclusion and/or use of non-automotive qualified products in automotive equipment or applications.

In the event that customer uses the product for design-in and use in automotive applications to automotive specifications and standards, customer (a) shall use the product without NXP Semiconductors' warranty of the product for such automotive applications, use and specifications, and (b) whenever customer uses the product for automotive applications beyond NXP Semiconductors' specifications such use shall be solely at customer's own risk, and (c) customer fully indemnifies NXP Semiconductors for any liability, damages or failed product claims resulting from customer design and use of the product for automotive applications beyond NXP Semiconductors' standard warranty and NXP Semiconductors' product specifications.

HTML publications — An HTML version, if available, of this document is provided as a courtesy. Definitive information is contained in the applicable document in PDF format. If there is a discrepancy between the HTML document and the PDF document, the PDF document has priority.

Translations — A non-English (translated) version of a document, including the legal information in that document, is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

Security — Customer understands that all NXP products may be subject to unidentified vulnerabilities or may support established security standards or specifications with known limitations. Customer is responsible for the design and operation of its applications and products throughout their lifecycles to reduce the effect of these vulnerabilities on customer's applications and products. Customer's responsibility also extends to other open and/or proprietary technologies supported by NXP products for use in customer's applications. NXP accepts no liability for any vulnerability. Customer should regularly check security updates from NXP and follow up appropriately. Customer shall select products with security features that best meet rules, regulations, and standards of the intended application and make the ultimate design decisions regarding its products and is solely responsible for compliance with all legal, regulatory, and security related requirements concerning its products, regardless of any information or support that may be provided by NXP.

NXP has a Product Security Incident Response Team (PSIRT) (reachable at PSIRT@nxp.com) that manages the investigation, reporting, and solution release to security vulnerabilities of NXP products.

NXP B.V. — NXP B.V. is not an operating company and it does not distribute or sell products.

Trademarks

Notice: All referenced brands, product names, service names, and trademarks are the property of their respective owners.

NXP — wordmark and logo are trademarks of NXP B.V.

UG10327

All information provided in this document is subject to legal disclaimers.

© 2025 NXP B.V. All rights reserved.

MCX E31x Hardware Design Guide

AMBA, Arm, Arm7, Arm7TDMI, Arm9, Arm11, Artisan, big.LITTLE, Cordio, CoreLink, CoreSight, Cortex, DesignStart, DynamIQ, Jazelle, Keil, Mali, Mbed, Mbed Enabled, NEON, POP, RealView, SecurCore, Socrates, Thumb, TrustZone, ULINK, ULINK2, ULINK-ME, ULINK-PLUS, ULINKpro, µVision, Versatile — are trademarks and/or registered trademarks of Arm Limited (or its subsidiaries or affiliates) in the US and/or elsewhere. The related technology may be protected by any or all of patents, copyrights, designs and trade secrets. All rights reserved.

HDQFP — is a trademark of NXP B.V.

MCX E31x Hardware Design Guide

Contents

1	Introduction	2
2	Power system	2
2.1	MCX E31x power domains and	
	configurations	2
2.2	VDD_HV_A - main I/O and analog supply	
	voltage	
2.3	VREFH – ADC high reference voltage	5
2.4	VDD_HV_B - secondary I/O supply voltage	
2.5	V11 - core logic voltage supply (+1.1 V)	
2.6	V25 - flash memory supply (+2.5 V)	7
2.7	V15 - high-current logic supply voltage	
	(+1.5 V)	7
2.8	VSS and VREFL – Ground and ADC	
	reference low	
2.9	Bulk and decoupling capacitors	9
2.10	Power considerations	10
2.10.1	MCU power supply ramp rate	10
2.11	Pinout differences between MCX E31B -	
	172 HDQFP and MCX E317 - 172 HDQFP	11
3	Clock circuitry	13
3.1	EXTAL and XTAL pins	13
4	Debug and programming interface	14
4.1	RESET system	
4.2	External pin RESET	14
4.3	JTAG and TRACE interface	
5	Communication modules	15
5.1	CAN interface	16
5.2	Ethernet MAC interface	
6	Quad serial peripheral interface	
7	Unused pins	21
8	References	22
9	Acronyms	
10	Revision history	
	Legal information	24

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.